

Digital Logic and Design


Quiz 2

Reg No: _____
Time: 20 minutes

Name: _____

Section: _____
Marks: _____/20

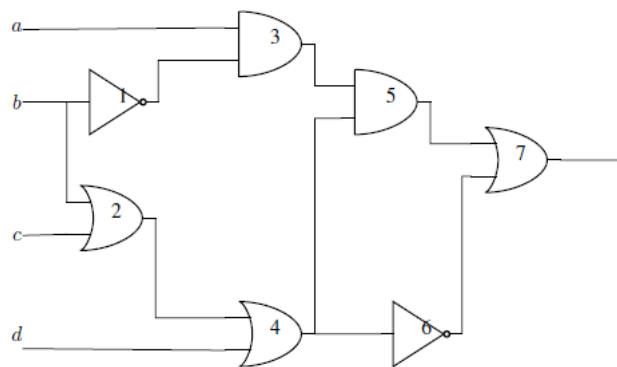Question 1: Convert given circuit to equivalent using NOR gates. (10)



Answer:

Take your answer from the previous question and complete wiring using ICs 74LS02. (10)

