

DIGITAL LOGIC & DESIGN (EE-1005)

ASSIGNMENT #4

ID: _____

NAME: _____

SECTION: _____

Read the Instructions Carefully NO Marks will be given if you failed to follow instructions

❖ Your assigned number is given to you in excel sheet provided with the assignment **FOR**

EXAMPLE: Assigned Number if your assigned number is **9846**

	Assign Digit 0	Assign Digit 1	Assign Digit 2	Assign Digit 3
Short for Assigned Digit	A0	A1	A2	A3
Write Assigned Number Digit By Digit	9	8	4	6


FOR EXAMPLE: Name is **HAMZA DAUD**

	ZERO CHARACTER OF YOUR NAME	FIRST CHARACTER OF YOUR NAME	SECOND CHARACTER OF YOUR NAME	THIRD CHARACTER OF YOUR NAME	FOURTH CHARACTER OF YOUR NAME
Short for CHARACTER	F0	F1	F2	F3	F4
YOUR NAME CHARACTER BY CHARACTER	H	A	M	Z	a
	ZERO CHARACTER OF YOURS SECOND NAME	FIRST CHARACTER OF YOUR SECOND NAME	SECOND CHARACTER OF YOUR SECOND NAME	THIRD CHARACTER OF YOUR SECOND NAME	FOURTH CHARACTER OF YOUR SECOND NAME
Short for CHARACTER	S0	S1	S2	S3	S4
YOUR NAME CHARACTER BY CHARACTER	D	@	U	d	z

1. Process the POSITIVE CLOCK EDGE JK FLIP FLOP circuit given below for all possible cases and fill the table accordingly?


CIRCUIT:

CLK=0

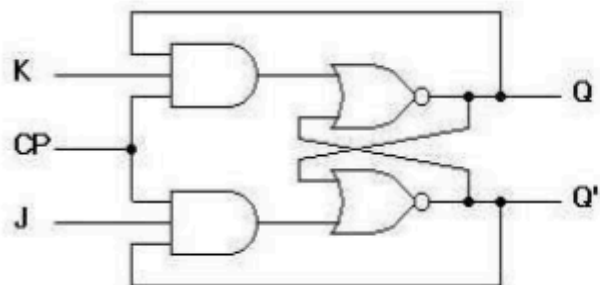


CASE I


J=0, K=0, Q=0

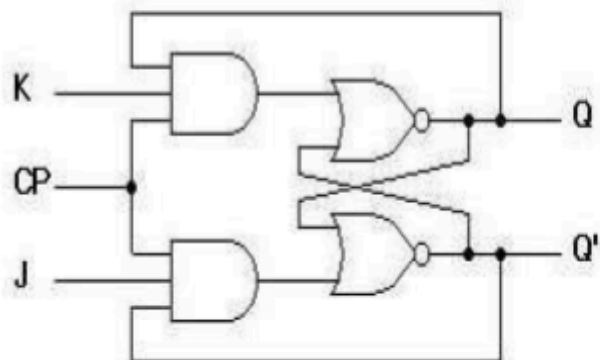

J=0, K=1, Q=0

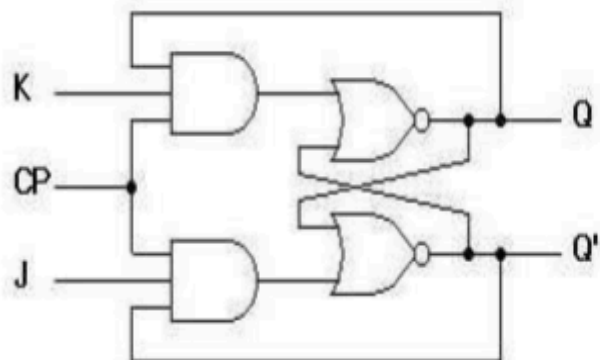


CLK=1

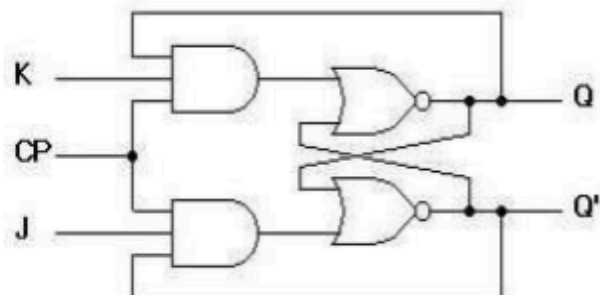


CASE-II


J=0, K=0, Q=1

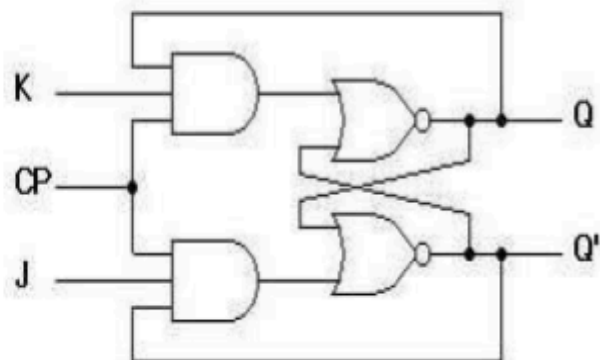


J=0, K=1, Q=1

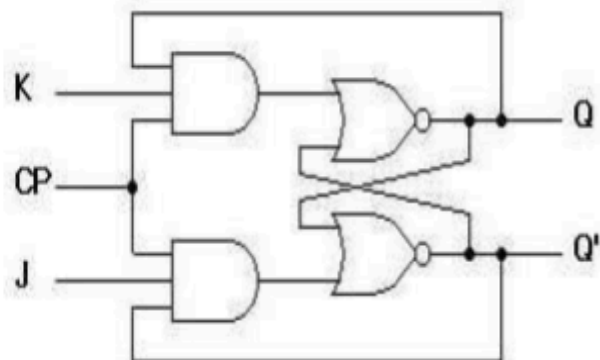


J=1,K=0,Q=0

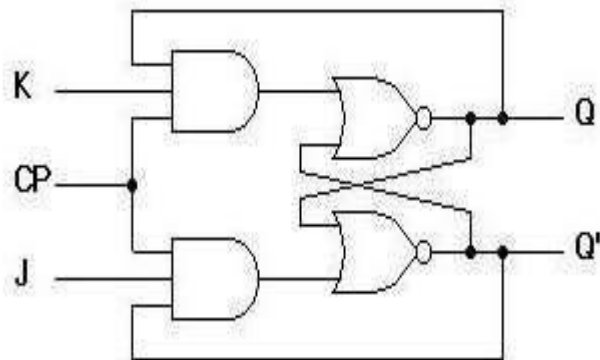

J=1,K=0,Q=1

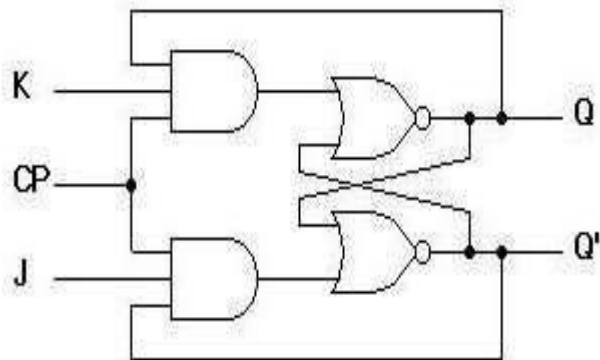

J=1,K=1,Q=0

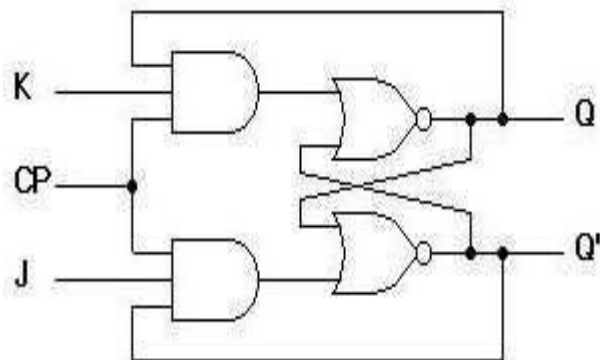

J=1,K=1,Q=1

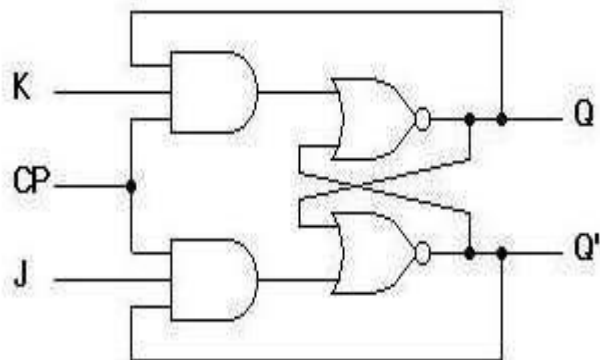


TABLE:

CLK	J	K	Q_{t+1}	\overline{Q}_{t+1}
0	X	X		
1	X	X		
↑	0	0		
↑	0	1		
↑	1	0		
↑	1	1		

2. Modify given circuit to introduce Asynchronous **CLEAR** and **SET** inputs fill table?
- HINT: For reference kindly read Section 7-2 of DIGITAL FUNDAMENTAL by Thomas Floyd, 10th Edition

CIRCUIT:

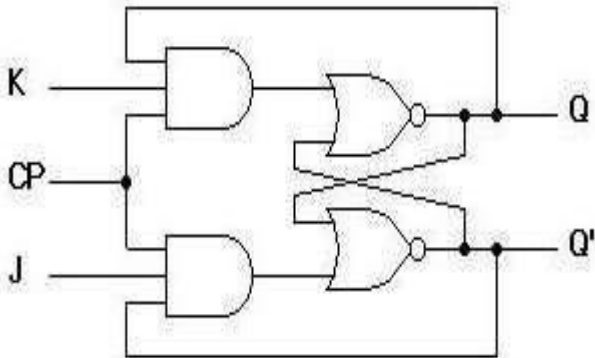


TABLE:

SET	CLEAR	Q_{t+1}	Q_{t+1}
0	0		
0	1		
1	0		
1	1		

3. For the given state table perform all of the following.

NOTE: Rename states in the table given below as $a = F0$, $b = S0$, $c = F1$, $d = S1$, $e = F2$, $f = S2$, $g = F3$, $h = S3$ and then perform following operations


✓ Draw the corresponding state diagram

TABLE:

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

STATE TRANSITION DIAGRAM:

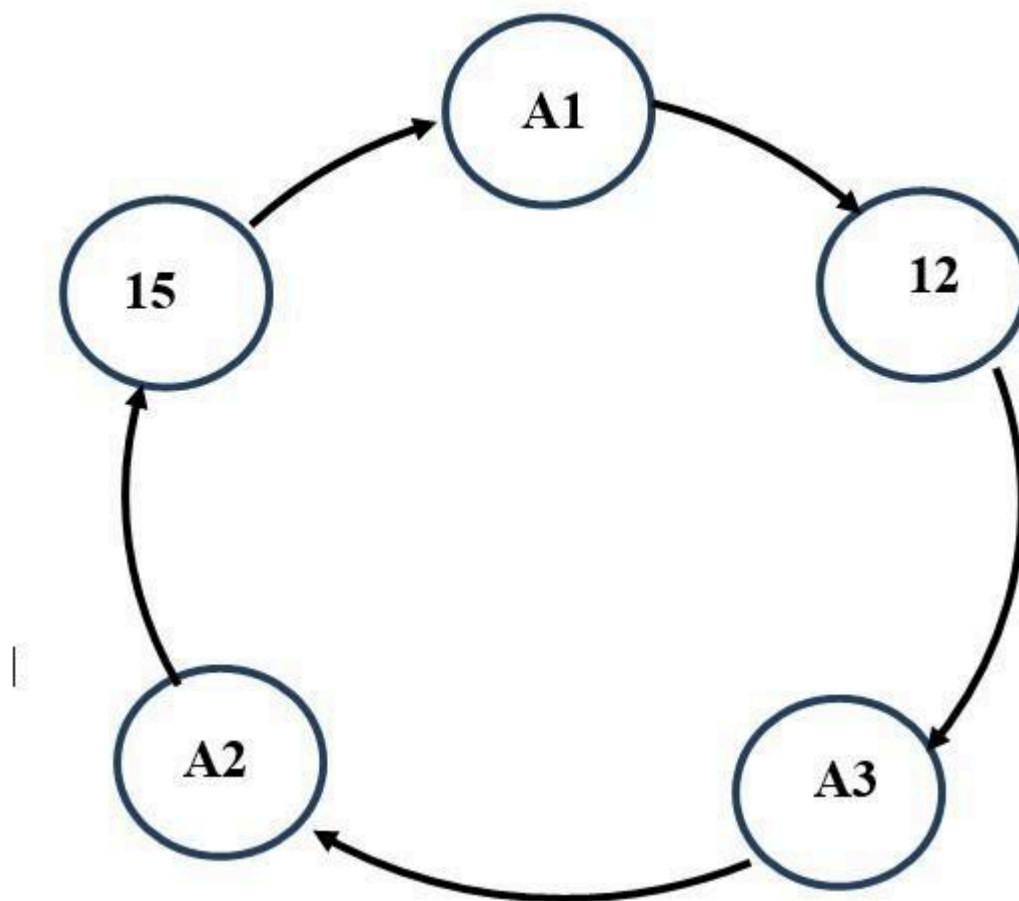4. Design circuit for given state diagram using T Flip-Flop?



TABLE, SIMPLIFICATION & EXPRESSIONS

5. Draw a three bit UP-DOWN Counter. For each bit you will have to use a different flip flop (JK, T, D). Follow the steps properly.

- State Diagram
- Next State Table
- State Reduction And Assignment
- Flip Flop Transition Table (FLIP FLOP Selection)
- Simplification
- Input/output Equations
- Implementations of Equation(Logic Diagram)

To decide which flip flop to use for your counter is based on your assigned number. Assume that $JK < T < D$. This means JK is the smallest, T flip flop is middle one and D flip flop is biggest one. Now based on the first 3 digits of your assigned number you will decide the pattern. For example, the id assigned number is **9486**, then pick the first three digits like 948. Since the first digit is the biggest so D flip flop should be used first. 4 is the smallest, so JK should be used in the middle and T flip flop should be used in the end.

