

# Digital Logic and Design


## Quiz 2

Reg No: \_\_\_\_\_  
Time: 20 minutes

Name: \_\_\_\_\_

Section: \_\_\_\_\_  
Marks: \_\_\_\_\_/20

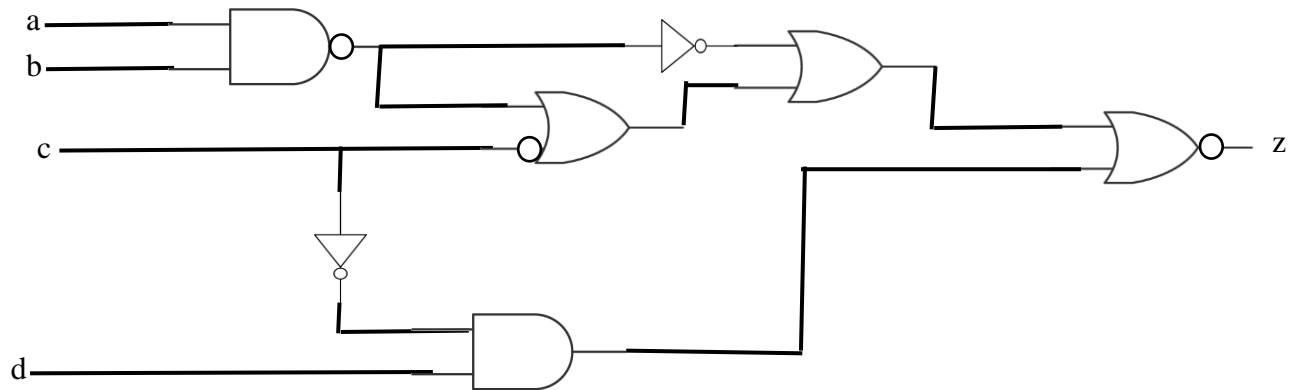Question 1: Convert given circuit to equivalent using NAND gates. (10)



**Answer:**

**Question 2:** Take your answer from the previous question and complete wiring using ICs 74LS02.  
(10)

