

DIGITAL LOGIC & DESIGN (EE-1005)

ASSIGNMENT #4

ID: 23i-2623

NAME: Muneeb Lone

SECTION: B

Read the Instructions Carefully NO Marks will be given if you failed to follow instructions

❖ Your assigned number is given to you in excel sheet provided with the assignment FOR

EXAMPLE: Assigned Number if your assigned number is 9846

| | Assign Digit 0 | Assign Digit 1 | Assign Digit 2 | Assign Digit 3 |
|--------------------------------------|----------------|----------------|----------------|----------------|
| Short for Assigned Digit | A0 | A1 | A2 | A3 |
| Write Assigned Number Digit By Digit | 7 | 6 | 5 | 0 |

FOR EXAMPLE: Name is HAMZA DAUD

| | ZERO CHARACTER OF YOUR NAME | FIRST CHARACTER OF YOUR NAME | SECOND CHARACTER OF YOUR NAME | THIRD CHARACTER OF YOUR NAME | FOURTH CHARACTER OF YOUR NAME |
|----------------------------------|-------------------------------------|-------------------------------------|--------------------------------------|-------------------------------------|--------------------------------------|
| Short for CHARACTER | F0 | F1 | F2 | F3 | F4 |
| YOUR NAME CHARACTER BY CHARACTER | M | U | N | E | e |
| | ZERO CHARACTER OF YOURS SECOND NAME | FIRST CHARACTER OF YOUR SECOND NAME | SECOND CHARACTER OF YOUR SECOND NAME | THIRD CHARACTER OF YOUR SECOND NAME | FOURTH CHARACTER OF YOUR SECOND NAME |
| Short for CHARACTER | S0 | S1 | S2 | S3 | S4 |
| YOUR NAME CHARACTER BY CHARACTER | L | 0 | n | 3E | |

ID: _____


ASSIGNMENT # 4 [EE-227]

Assigned Number: _____

1. Process the POSITIVE CLOCK EDGE JK FLIP FLOP circuit given below for all possible cases and fill the table accordingly?


CIRCUIT:

CLK=0

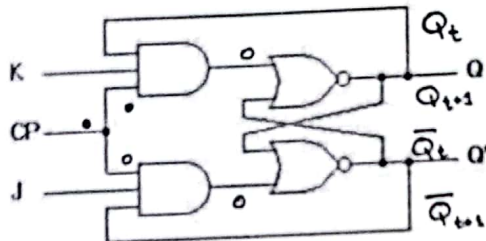


CASE I


J=0, K=0, Q=0

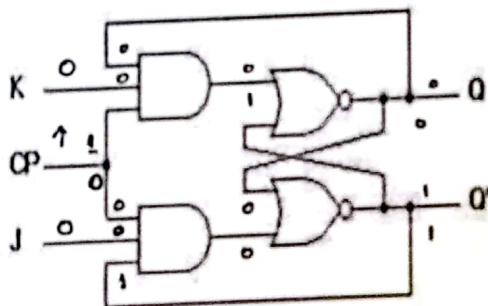

J=0, K=1, Q=0

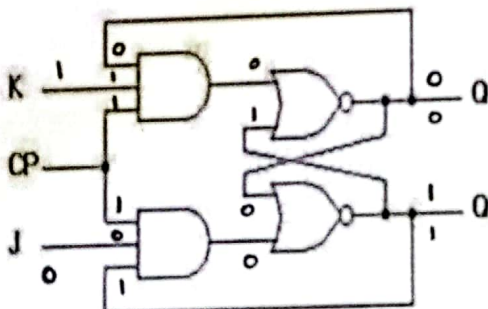


CLK=1

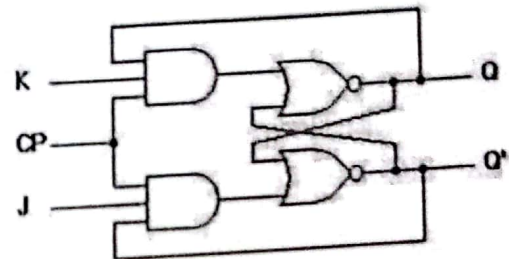


CASE-II

J=0, K=0, Q=1

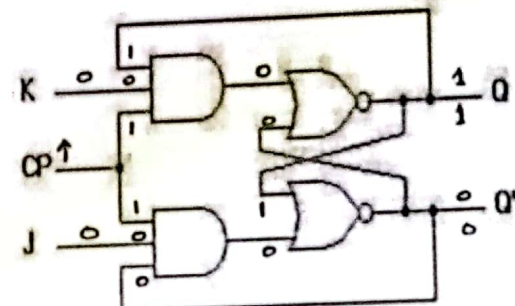

J=0, K=1, Q=1

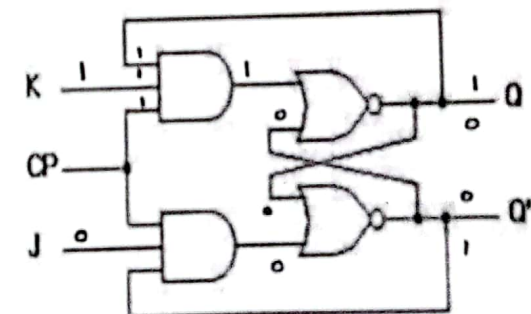

ID: _____

ASSIGNMENT # 4 [EE-227]

Assigned Number: _____

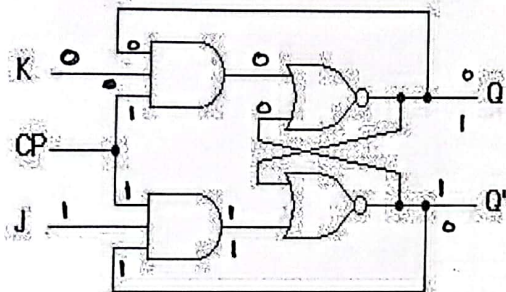
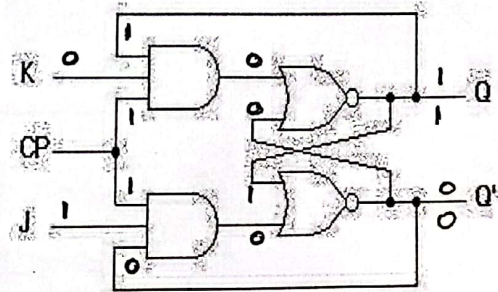
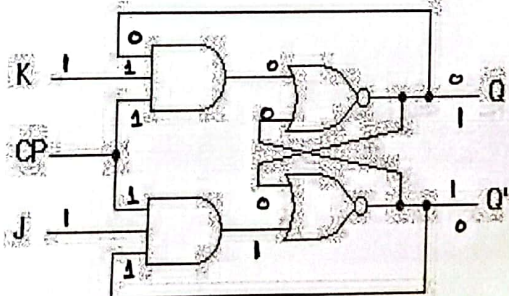
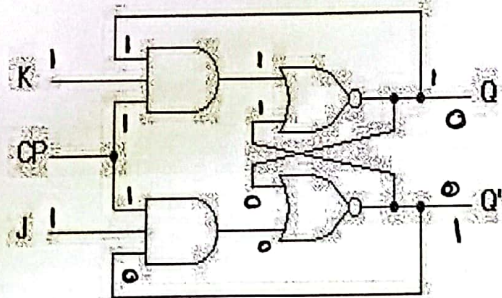
 $J=1, K=0, Q=0$  $J=1, K=0, Q=1$  $J=1, K=1, Q=0$  $J=1, K=1, Q=1$ 

TABLE:

| CLK | J | K | Q_{t+1} | \overline{Q}_{t+1} |
|-----|---|---|------------------|----------------------|
| 0 | X | X | Q_t | \overline{Q}_t |
| 1 | X | X | Q_t | \overline{Q}_t |
| ↑ | 0 | 0 | Q_t | \overline{Q}_t |
| ↑ | 0 | 1 | 0 | 1 |
| ↑ | 1 | 0 | 1 | 0 |
| ↑ | 1 | 1 | \overline{Q}_t | Q_t |

ID:

ASSIGNMENT # 4 [EE-227]

Assigned Number:

2. Modify given circuit to introduce Asynchronous CLEAR and SET inputs fill table?

HINT: For reference kindly read Section 7-2 of DIGITAL FUNDAMENTAL by Thomas Floyd, 10th Edition

CIRCUIT:

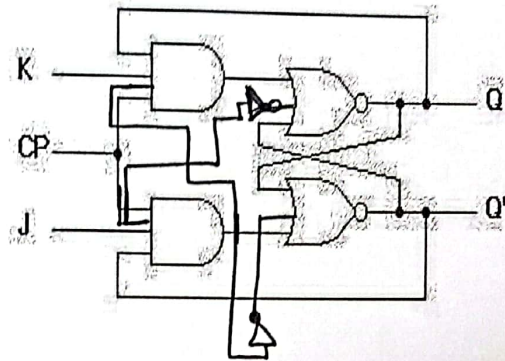


TABLE:

| SET | CLEAR | Q_{t+1} | Q'_{t+1} |
|-----|-------|----------------------|------------|
| 0 | 0 | invalid | invalid |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | Depends on JK Inputs | |

3. For the given state table perform all of the following.


NOTE: Rename states in the table given below as $a=F0$, $b=S0$, $c=F1$, $d=S1$, $e=F2$, $f=S2$, $g=F3$, $h=S3$ and then perform following operations

✓ Draw the corresponding state diagram

TABLE:

| Present State | Next State | | Output | |
|-------------------------|------------|-------|--------|-------|
| | $x=0$ | $x=1$ | $x=0$ | $x=1$ |
| $a \rightarrow M$ | f | b | 0 | 0 |
| $b \rightarrow L$ | d | c | 0 | 0 |
| $c \rightarrow U$ | f | e | 0 | 0 |
| $d \rightarrow O$ | g | a | 1 | 0 |
| $e \rightarrow N$ | d | c | 0 | 0 |
| $f \rightarrow \sim$ | f | b | 1 | 1 |
| $g \rightarrow E$ | g | h | 0 | 1 |
| $h \rightarrow \exists$ | g | a | 1 | 0 |

STATE TRANSITION DIAGRAM:

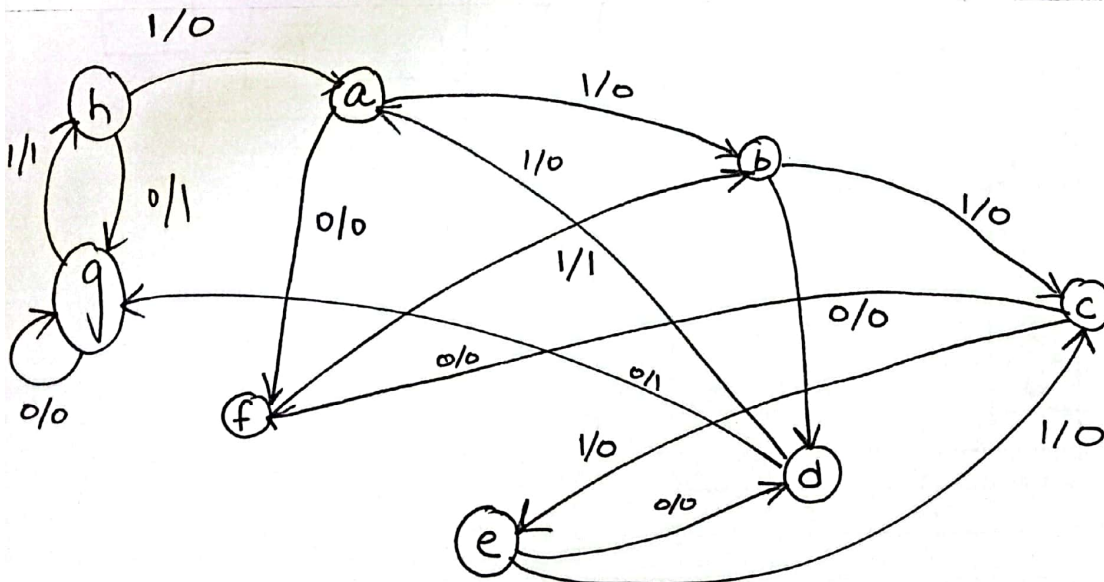


ID: _____

ASSIGNMENT # 4 [FF-1005]

Assigned Number: _____

4. Design circuit for given state diagram using T Flip-Flop?

| Q_t | Q_{t+1} | T |
|-------|-----------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

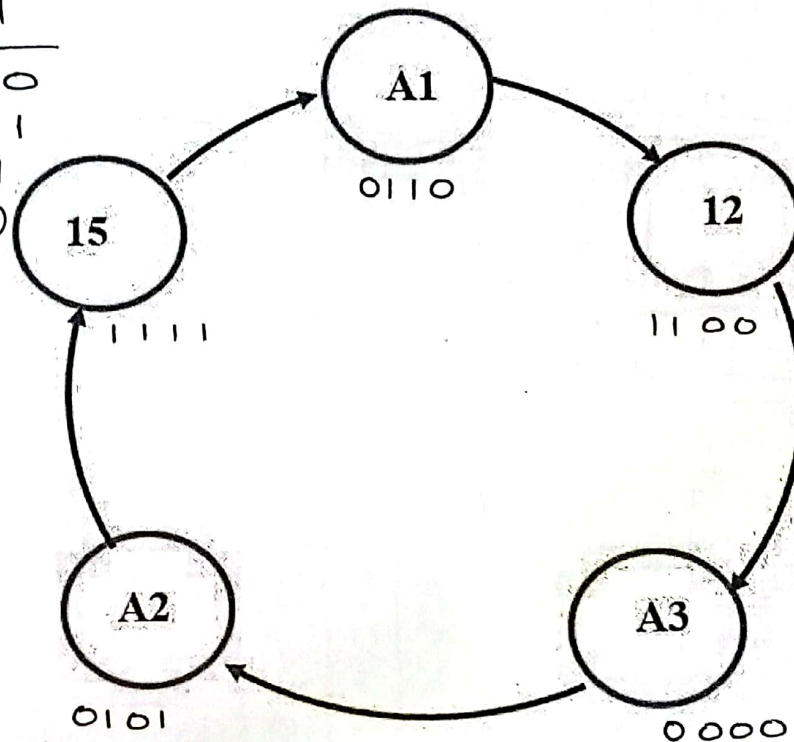TABLE, SIMPLIFICATION & EXPRESSIONS
Current Stage Stage Next & Inputs

| | A ₀ | B ₀ | C ₀ | D ₀ | A | B | C | D | I _A | I _B | I _C | I _D |
|----|----------------|----------------|----------------|----------------|---|---|---|---|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | x | x | x | x | x | x | x | x |
| 2 | 0 | 0 | 1 | 0 | x | x | x | x | x | x | x | x |
| 3 | 0 | 0 | 1 | 1 | x | x | x | x | x | x | x | x |
| 4 | 0 | 1 | 0 | 0 | x | x | x | x | x | x | x | x |
| 5 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 6 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 | x | x | x | x | x | x | x | x |
| 8 | 1 | 0 | 0 | 0 | x | x | x | x | x | x | x | x |
| 9 | 1 | 0 | 0 | 1 | x | x | x | x | x | x | x | x |
| 10 | 1 | 0 | 1 | 0 | x | x | x | x | x | x | x | x |
| 11 | 1 | 0 | 1 | 1 | x | x | x | x | x | x | x | x |
| 12 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 | x | x | x | x | x | x | x | x |
| 14 | 1 | 1 | 1 | 0 | x | x | x | x | x | x | x | x |
| 15 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |

I_A

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | x | x | x |
| 01 | x | 1 | x | 1 |
| 11 | 1 | x | 1 | x |
| 10 | x | x | x | x |

$$I_A = B$$

I_B

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 1 | x | x | x |
| 01 | x | 0 | x | 0 |
| 11 | 1 | x | 0 | x |
| 10 | x | x | 1 | x |

$$I_B = \bar{B} + B\bar{C}\bar{D}$$

I_C


| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | x | x | x |
| 01 | x | 1 | x | 1 |
| 11 | 0 | x | 0 | x |
| 10 | x | x | x | x |

$$I_C = \bar{A}B$$

I_D

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 1 | x | x | x |
| 01 | x | 0 | x | 0 |
| 11 | 0 | x | 1 | x |
| 10 | x | x | x | x |


$$I_D = \bar{A}\bar{B} + AD$$

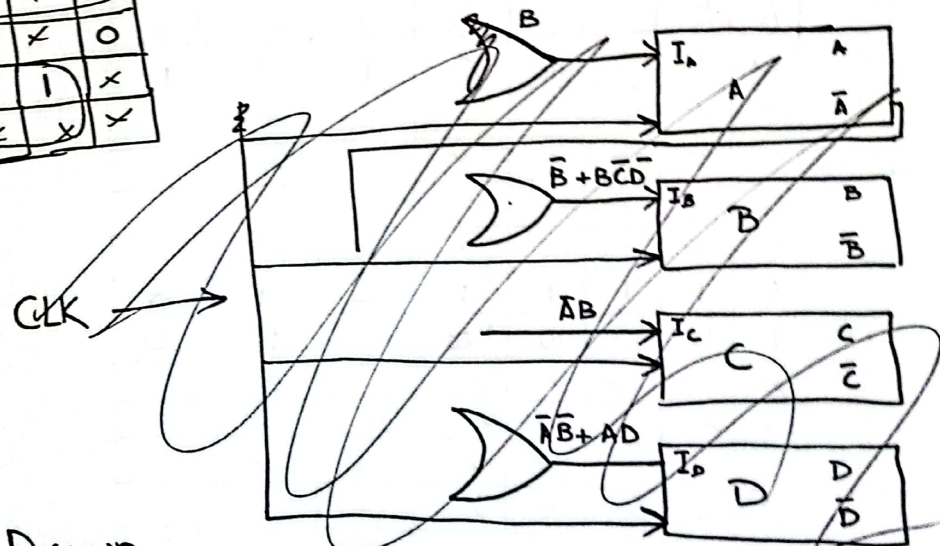

Drawn on previous page

$$I_A = B, I_B = \bar{B} + B\bar{C}\bar{D}, I_C = \bar{A}B, I_D = \bar{A}\bar{B} + AD$$

CLK

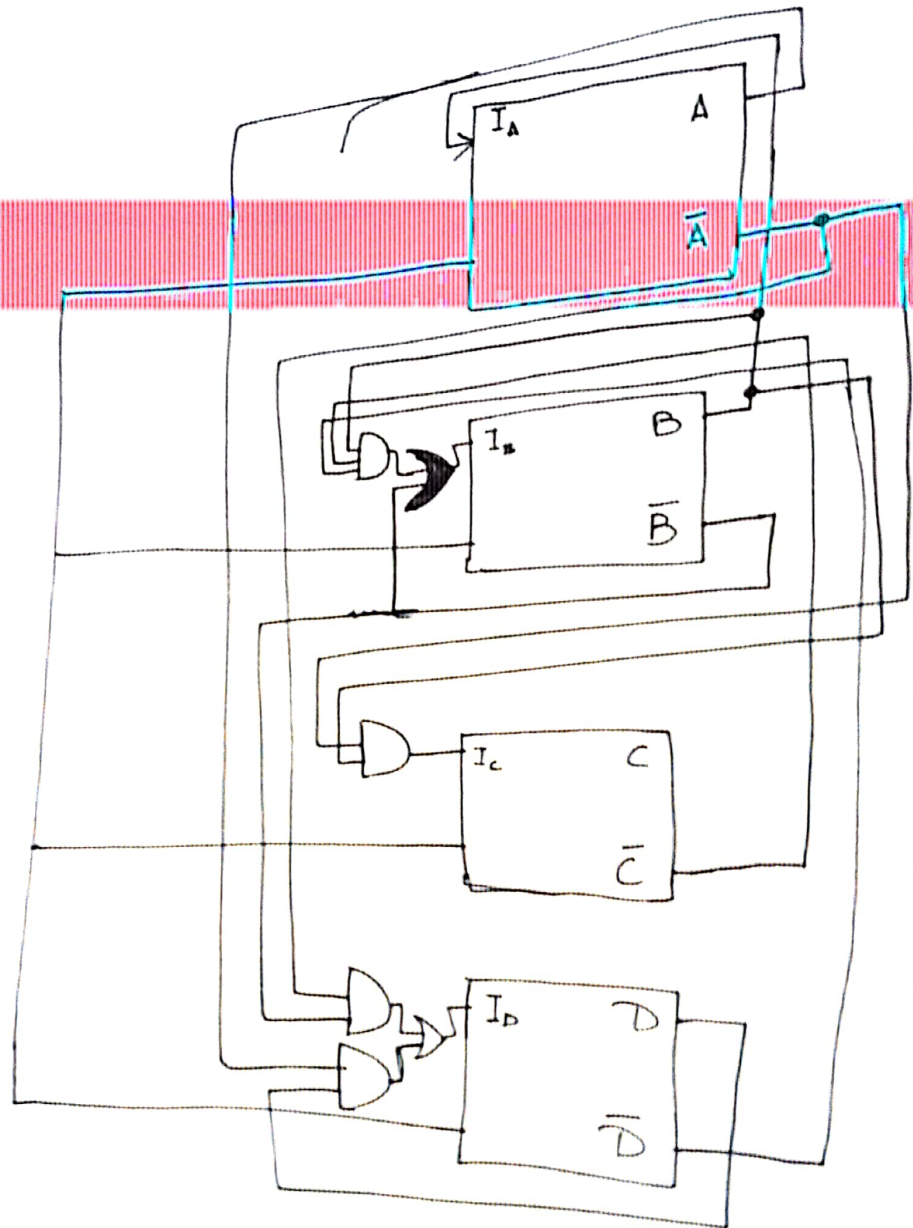

Draw a three bit UP-DOWN Counter. For each bit you will have to use a different flip flop (JK, T, D). Follow the steps properly.

765

D → T → JK

- State Diagram
- Next State Table
- State Reduction And Assignment
- Flip Flop Transition Table (FLIP FLOP Selection)
- Simplification
- Input/output Equations
- Implementations of Equation (Logic Diagram)

To decide which flip flop to use for your counter is based on your assigned number. Assume that $JK < T < D$. This means JK is the smallest, T flip flop is middle one and D flip flop is biggest one. Now based on the first 3 digits of your assigned number you will decide the pattern. For example, the assigned number is 9486, then pick the first three digits like 948. Since the first digit is the biggest so D flip flop should be used first. 4 is the smallest, so JK should be used in the middle and T flip flop should be used in the end.

Excitation Tables

| Q_t | Q_{t+1} | J | K |
|-------|-----------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

Truth Tables

| J | K | Q_{t+1} |
|---|---|------------------|
| 0 | 0 | Q_t |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | $\overline{Q_t}$ |

| Q_t | Q_{t+1} | D |
|-------|-----------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| D | Q_{t+1} | $\overline{Q_{t+1}}$ |
|---|-----------|----------------------|
| 0 | 0 | 1 |
| 1 | 1 | 0 |

| Q_t | Q_{t+1} | T |
|-------|-----------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| T | Q_{t+1} |
|---|------------------|
| 0 | Q_t |
| 1 | $\overline{Q_t}$ |

A sequential circuit shown in the given figure has three D flip-flops D_0 , D_1 and D_2 , two inputs X and Y , and outputs Z_1 and Z_2 .

- ✓ Derive the STATE EQUATIONS
- ✓ Tabulate the STATE TABLE.
- ✓ Draw the STATE DIAGRAM of the circuit

